



2EC501-VLSI DESIGN
SPECIAL ASSIGNMENT

TOPIC: 2 Bit binary to Gray code converter

Submitted by:

NAME	ROLL NO.
CHIRAG RAJWANI	21BEC021

Submitted to:

Prof. Usha Mehta

Prof. Jayesh Patel

Department of Electronics & Communications Engineering, IT-NU


❖ **GATE LEVEL circuit diagram & Boolean equation for 2 bit binary to Gray code converter:-**

Binary	Gray
--------	------

B0	B1	G0	G1
0	0	0	0
1	0	1	0
0	1	1	1
1	1	0	1

- ❖ To find the corresponding digital circuit, I will use the K-Map technique for each of the Gray code bits as output with all of the binary bits as input;

For G0 →

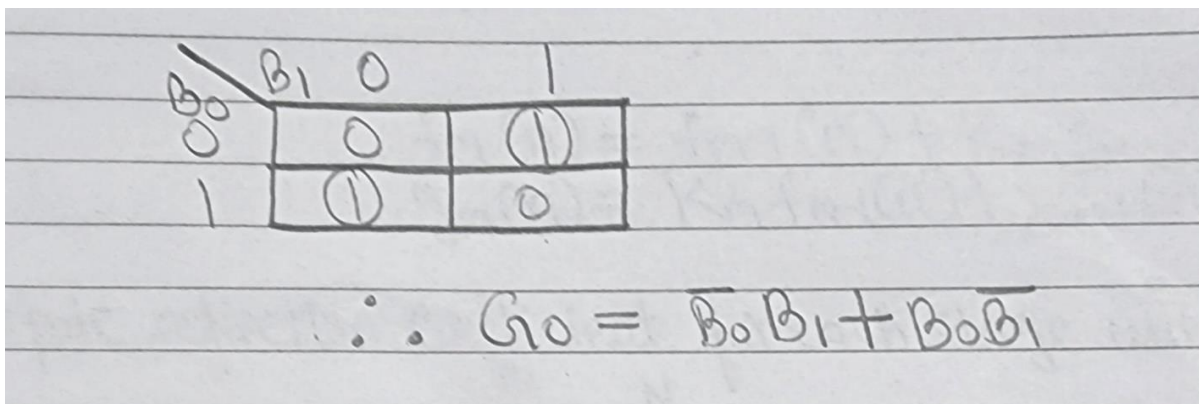

A handwritten K-map for the Gray code bit G0. The K-map is a 2x2 grid. The columns are labeled B1 (0, 1) and the rows are labeled B0 (0, 1). The values in the cells are: (B1=0, B0=0) is 0; (B1=1, B0=0) is 1; (B1=0, B0=1) is 1; (B1=1, B0=1) is 0. Below the K-map, the Boolean equation is written as $G_0 = \overline{B_0}B_1 + B_0\overline{B_1}$.


$$\therefore G_0 = \overline{B_0}B_1 + B_0\overline{B_1}$$

For G1 →

$B_0 \backslash B_1$	0	1
0	0	1
1	0	1

$$\therefore G_1 = \overline{B_0} B_1 + B_0 B_1$$
$$= B_1 (B_0 + \overline{B_0})$$
$$= B_1$$

 Therefore the optimized gate level circuit diagram obtained is:-



❖ Now the transistor level schematic diagram for a CMOS inverter circuit implementation is to be drawn, requiring;

➤ Optimized calculation for total no. of transistors to be used:

Total number of inputs to be given into the circuit;

• B0

• B1


• B0



• B1

And also assuming that both the inputs are only available in normal form and none is available in complement form.

Thus, 4 transistors are required for the mentioned four inputs each in pull up & pull down network, alongside which 4 extra transistors are required as to form an inverter for attaining the complemented form.

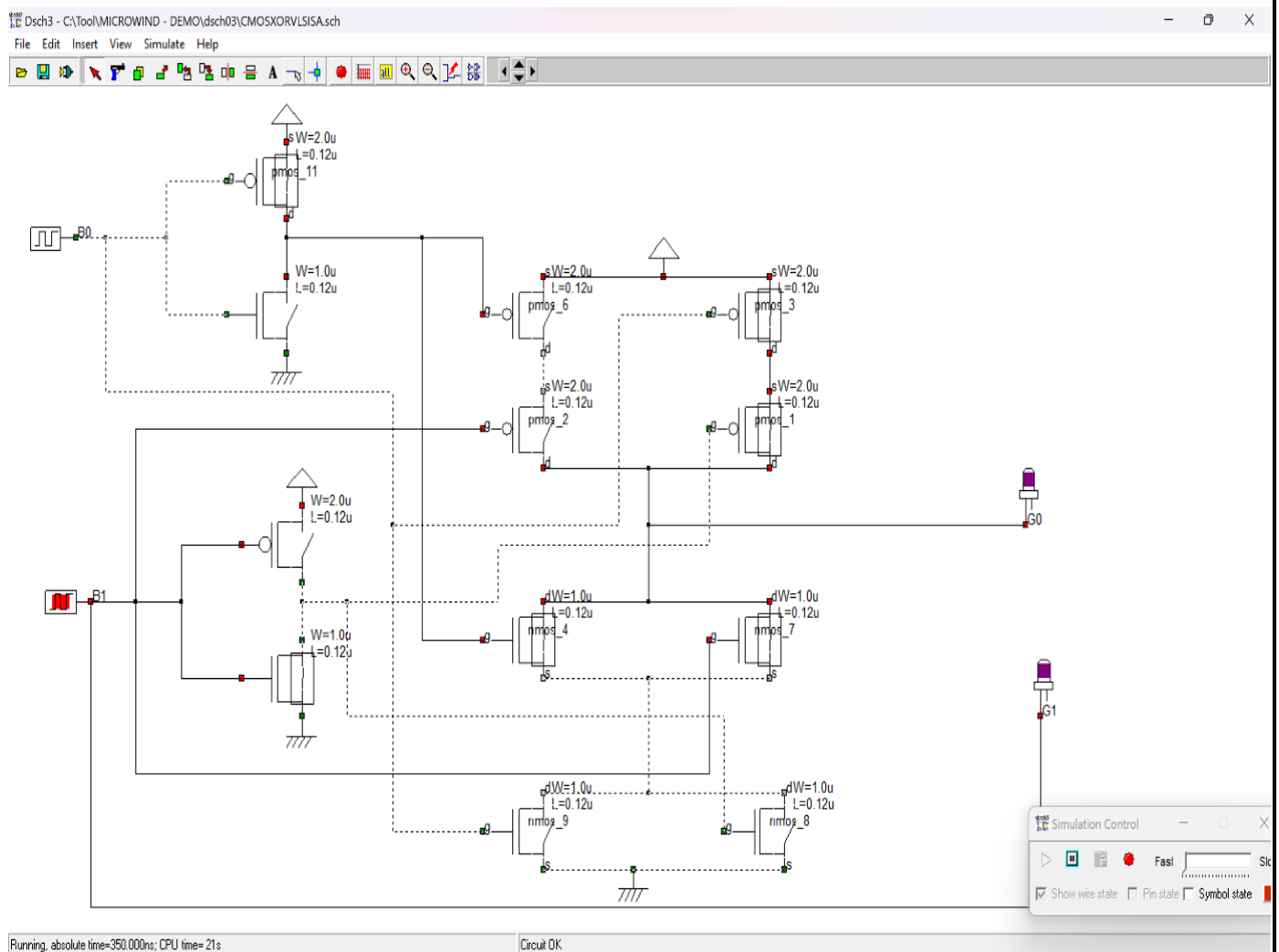
Therefore, 12 transistors are required in total to fabricate the transistor level schematic, such as;



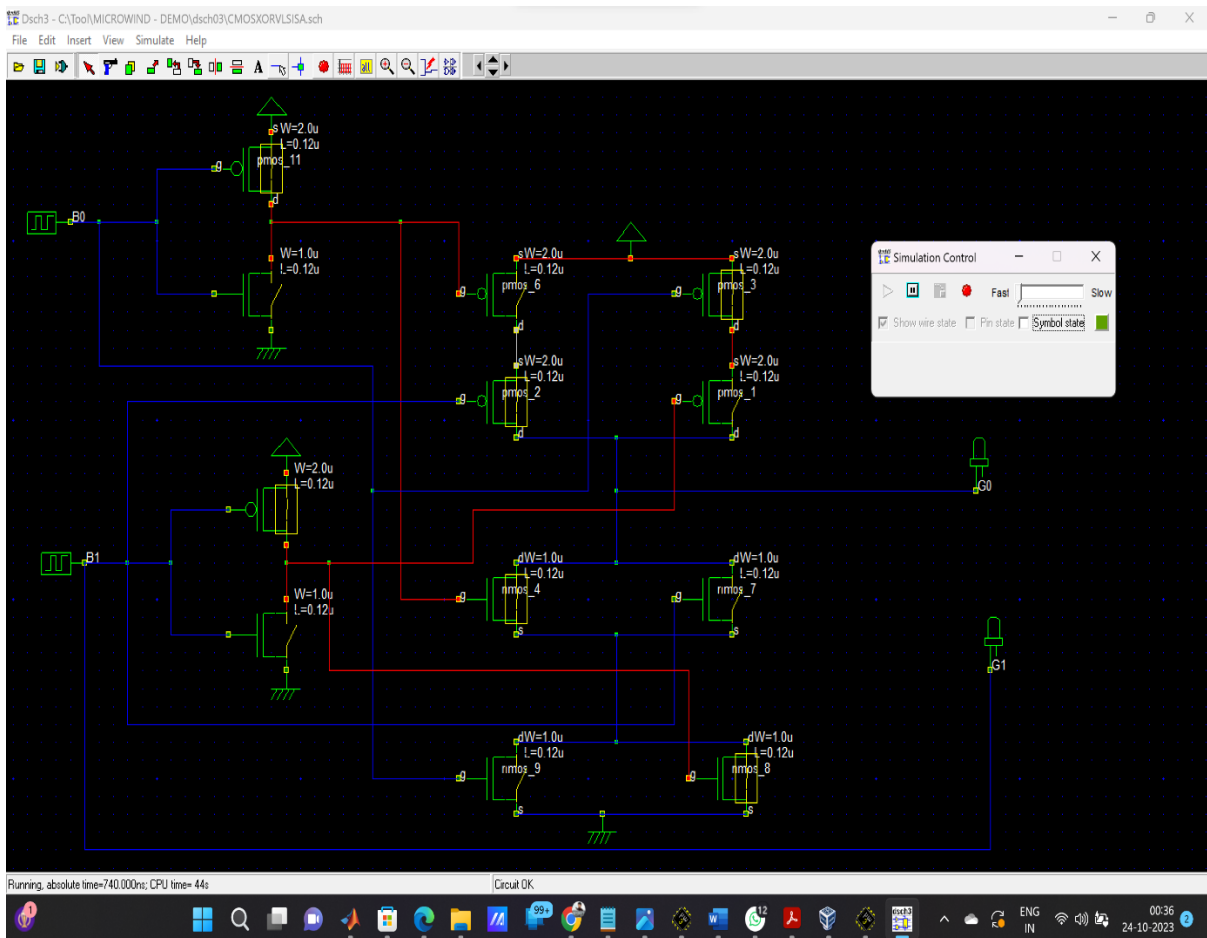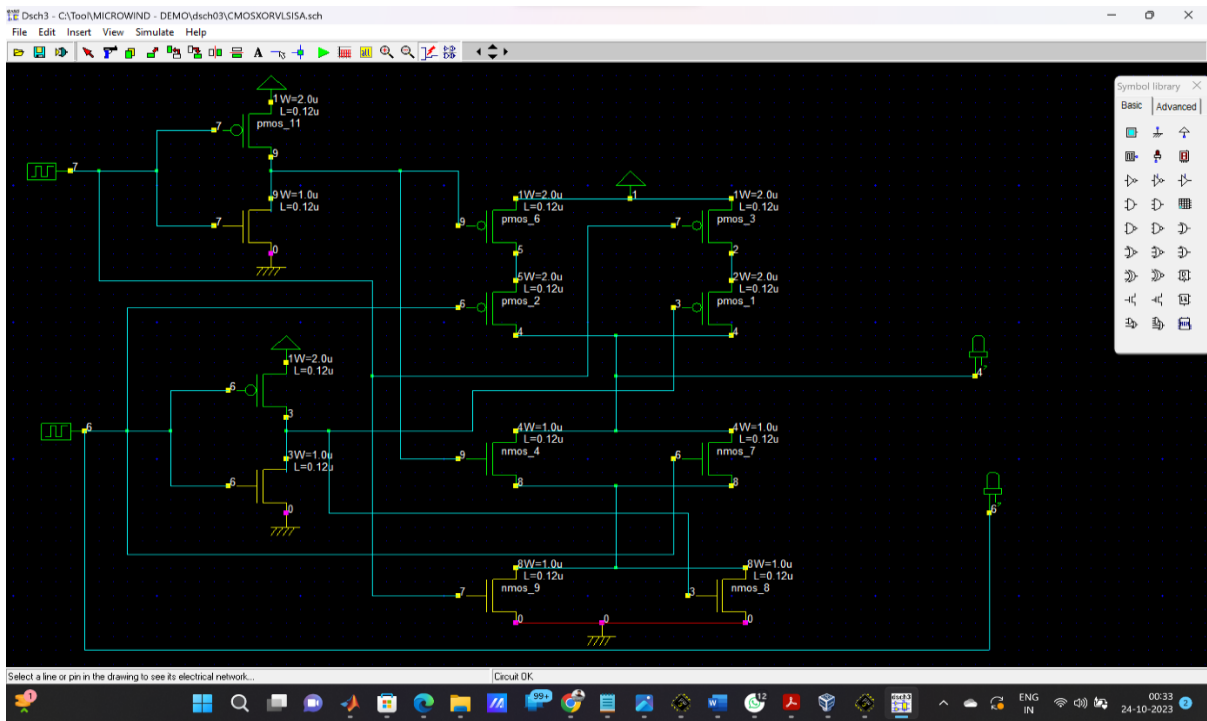



Timing diagrams of C:\Tool\MICROWIND - DEMO\dsch03\CMOSBINTOGRAYVLSISA2.sch

Chrono View All Options

 

Timing diagrams of C:\Tool\MICROWIND - DEMO\dsch03\CMOSBINTOGRAYVLSISA2.sch


Chrono View All Options

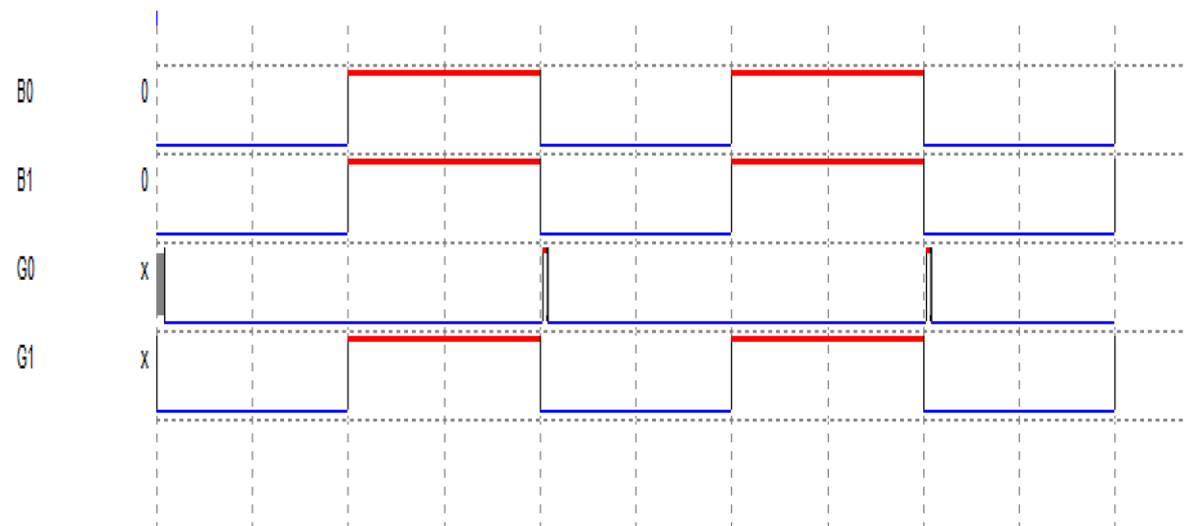 

❖ Stick diagram for the same could be drawn out in the following manner :-


Colour code being followed is as shown below →

Part	Color
PMOS	Yellow
NMOS	Green
GND, Vdd	Blue
Inputs	Red
Connectors	Dot

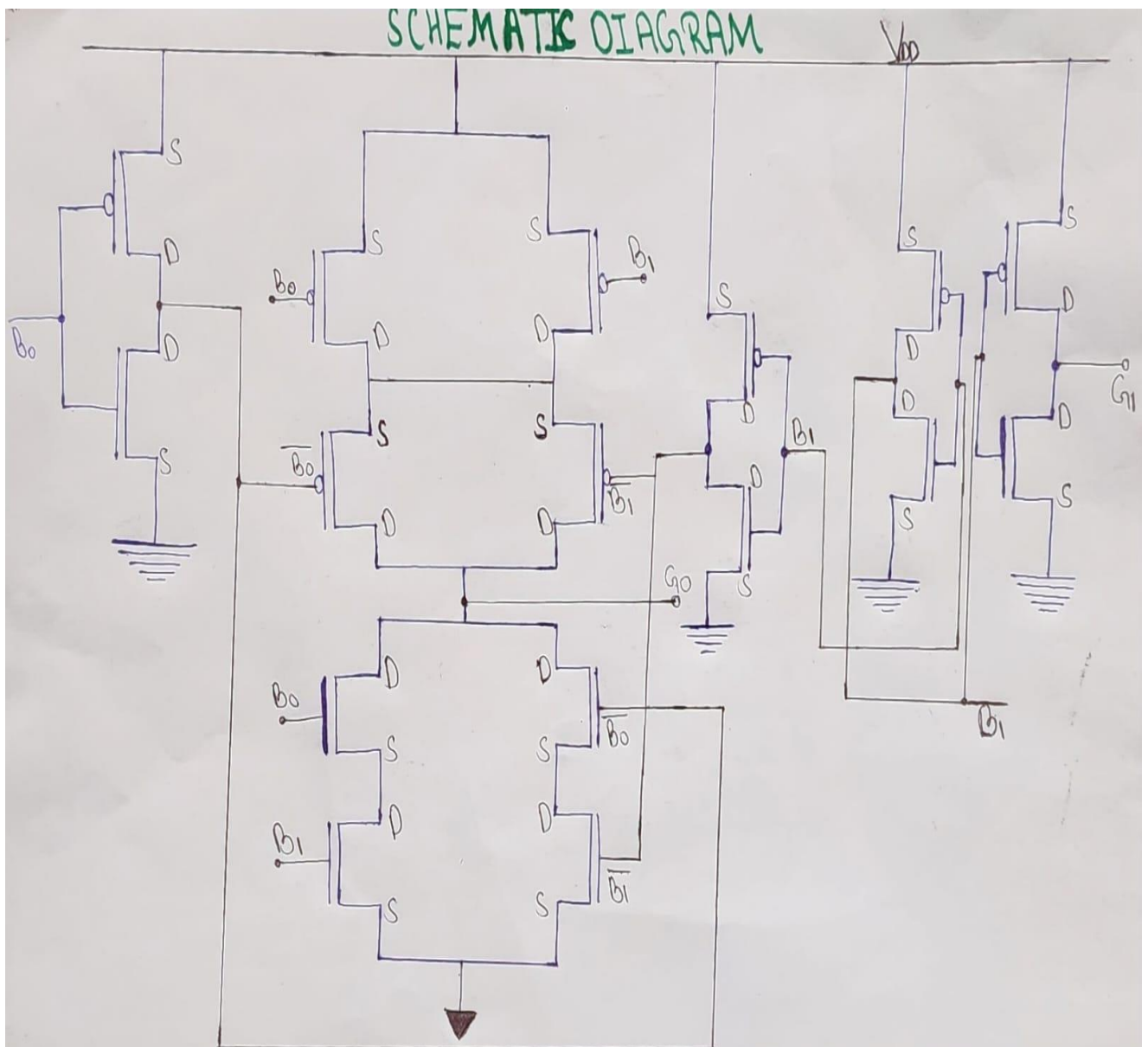



EULER'S PATH

Pull up Network

 

COMMON PATH :- $B_0 B_1 \bar{B}_1 \bar{B}_0$

Pull down Network

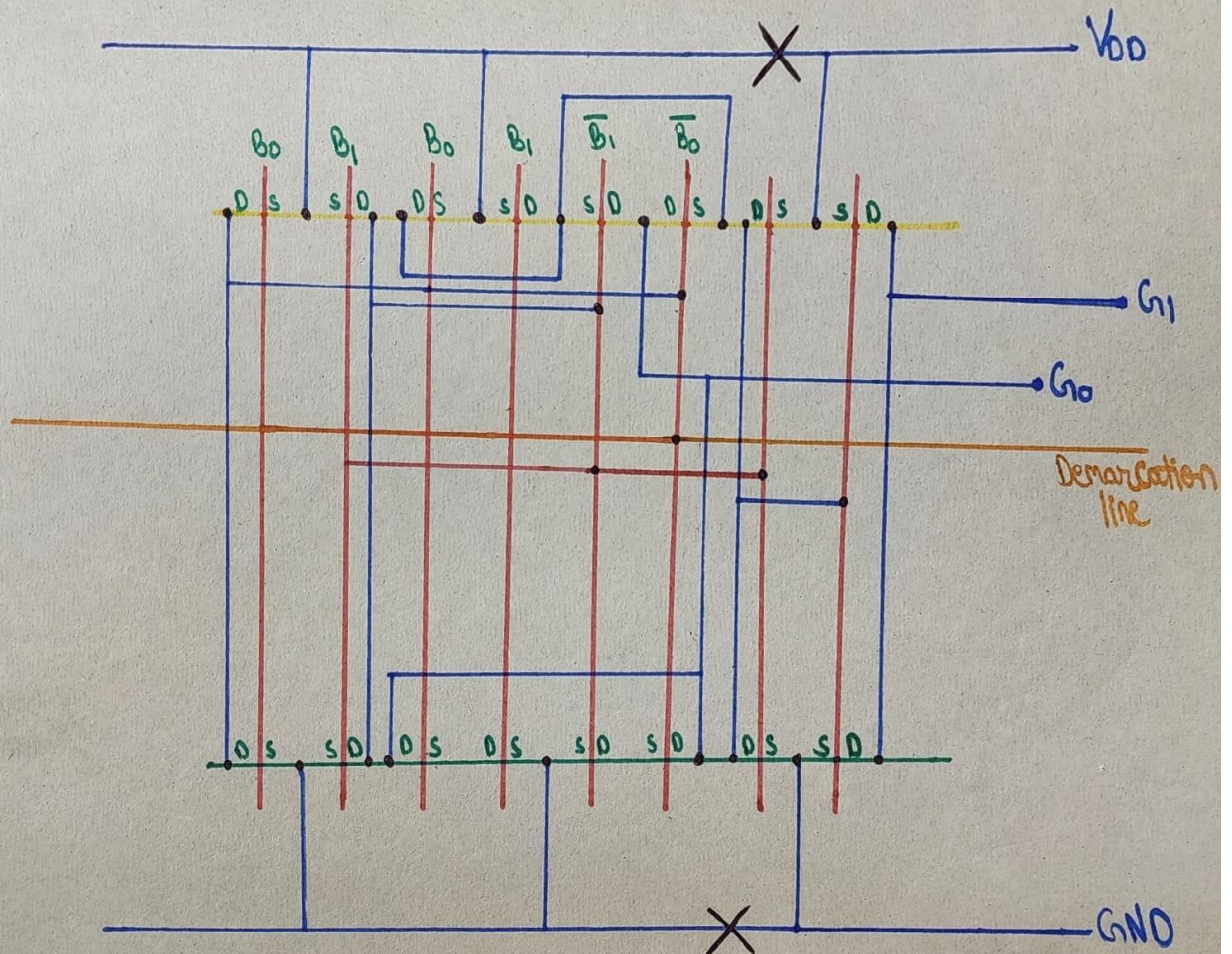 

- ❖ State the various levels of ***VOL*** corresponding to various transistor states.

ANS. The levels of voltage (VOH and VOL) for each transistor state would depend on the specific technology used, but generally, they would correspond to logical high (1) and logical low (0) levels for the binary and Gray code values. Here is a basic representation of the transistor states for a 2-bit binary to Gray code converter:

Binary input	Gray output	Transistor 1	Transistor 2
00	00	OFF (Vol)	OFF(Vol)
01	01	ON(Voh)	OFF(Vol)
10	11	OFF(Vol)	ON(Voh)
11	10	ON(Voh)	ON(Voh)

Here, Vol is the low voltage level (logical 0). When Transistor 1 is ON, it represents a binary 1, and when it's OFF, it represents a binary 0. Similarly, Transistor 2 represents the second bit's state in the binary code.

- ❖ Find the equivalent CMOS inverter circuit.

→ In the circuit which I have designed; for the optimum output, the (W/L)equivalents for PMOS & NMOS are as follows respectively:-

$$(W/L)_{eq.} = (140\lambda / 6\lambda) = (14 * 0.600 / 6 * 0.06) \mu m$$

$$(W/L)_{pmos} = (78\lambda / 6\lambda) = (7.8 * 0.600 / 6 * 0.06) \mu m$$

$$(W/L)_{nmos} = (62\lambda / 6\lambda) = (6.2 * 0.600 / 6 * 0.06) \mu m$$

Therefore, $(W/L)_{pmos} = \underline{\underline{0.5571(W/L)_{eq.}}}$
 $(W/L)_{nmos} = \underline{\underline{0.4428(W/L)_{eq.}}}$

- ❖ For CMOS/MOS implementation, which input patterns give the lowest output resistance when output is low? What is the value of that resistance?

ANS. For the following input patterns output is low:-

B0	B1	G0
1	1	0
0	0	0

Here, in both the cases assuming that the transistors have been sized to give a worst-case output resistance of $20\text{ K}\Omega$; the lowest output resistance turns out to be **$80\text{ K}\Omega$** .

And, in case of G1; the lowest output resistance turns out to be **$20\text{ K}\Omega$** for the input pattern of $B1=0$, for which G1 is low.

- ❖ For CMOS/MOS implementation, which input patterns give the lowest output resistance when output is low? What is the value of that resistance?

ANS. For the following input patterns output is high :-

B0	B1	G0
1	0	1
0	1	1


Here, in both the cases assuming that the transistors have been sized to give a worst-case output resistance of $20\text{ K}\Omega$; the lowest output resistance turns out to be **$20\text{ K}\Omega$** .

And, in case of G1 also; the lowest output resistance turns out to be **$20\text{ K}\Omega$** for the input pattern of $B1=1$, for which G1 is high.

❖ Prepare the layout using MICROWIND tool.

10 lambda
0.600µm

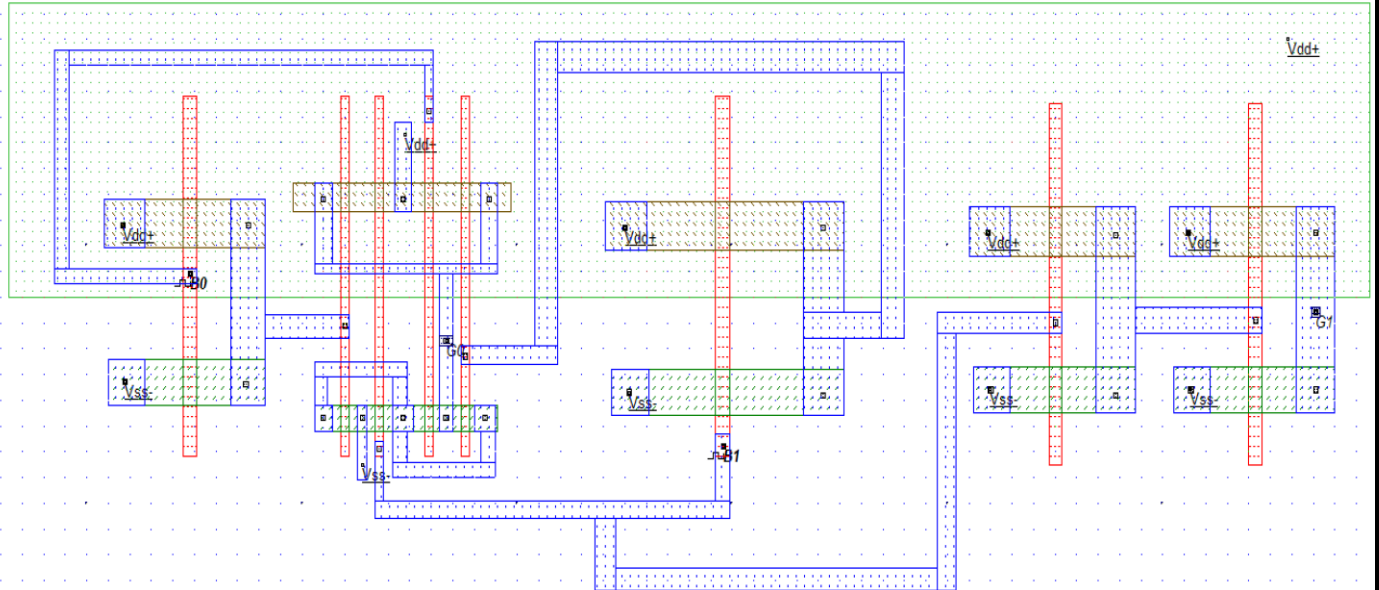21BEC021 2BIT BINARY TO GRAY CODE CONVERTER




5.00ns simulation in 4s, with MOS model Level 3 with 8 NMOS, 8 pMOS

N5 Vdd

CMOS 0.12µm - 6 Metal (1.20V,2.50V)

10 lambda
0.600µm

 21BEC021 2BIT BINARY TO GRAY CODE CONVERTER




5.00ns simulation in 4s, with MOS model Level 3 with 8 NMOS, 8 pMOS


Temperature 27.0°C

CMOS 0.12µm - 6 Metal (1.20V,2.50V)

 ❖ Simulate it for various combinations of inputs.




 ✚ 2 bit Binary to Gray code converter for $V_{in}=1.2V$




2 bit Binary to Gray code converter for $V_{in} = 1.8V$

 Analog simulation of C:\Tool\MICROWIND - DEMO\mw03\21BEC021 2BIT BINARY TO GRAY CODE CONVERTER.MSK




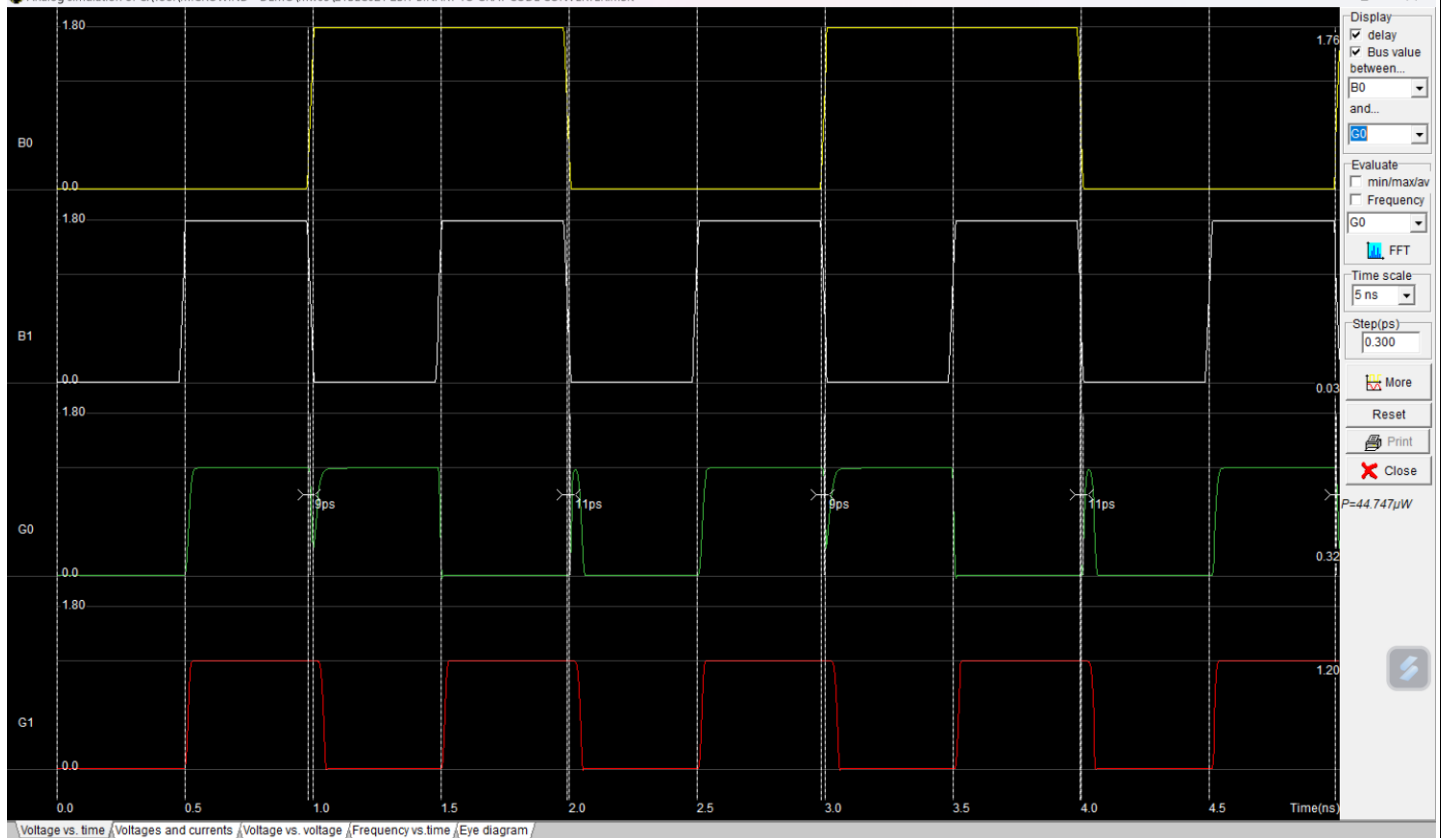Analog simulation of C:\Tool\MICROWIND - DEMO\mw03\21BEC021 2BIT BINARY TO GRAY CODE CONVERTER.MSK




2bit Binary to Gray code converter for $V_{in} = 2.5V$

 
Analog simulation of C:\Tool\MICROWIND - DEMO\mw03\21BEC021 2BIT BINARY TO GRAY CODE CONVERTER.MSK



 
Analog simulation of C:\Tool\MICROWIND - DEMO\mw03\21BEC021 2BIT BINARY TO GRAY CODE CONVERTER.MSK




❖ Measure the rise time, fall time, propagation delay and other parameters.

 For $V = 1.2V$

W/L PMOS (μm)	W/L NMOS (μm)	τ_{pHL} (ps)	τ_{pLH} (ps)
<u>0.78</u>	<u>0.62</u>	<u>11</u>	<u>13</u>

 For $V = 1.8V$

W/L PMOS (μm)	W/L NMOS (μm)	τ_{pHL} (ps)	τ_{pLH} (ps)
<u>0.78</u>	<u>0.62</u>	<u>9</u>	<u>11</u>

 For $V = 2.5V$

W/L PMOS (μm)	W/L NMOS (μm)	τ_{pHL} (ps)	τ_{pLH} (ps)
<u>0.78</u>	<u>0.62</u>	<u>8</u>	<u>11</u>

❖ CONCLUSION :-

- Gray Code system is a binary number system in which every successive pair of numbers differs in only one bit. It is used in applications in which the normal sequence of binary numbers generated by the hardware may produce an error or ambiguity during the transition from one number to the next bit and from here, the significance of a Binary to Gray code converter could be derived.

- The different V values for different input patterns were observed, and it was noticed that the path including the NMOS offers the least resistance. Furthermore, the higher the input source voltage, the better the obtained characteristics.
- Some of the furthermore applications of the developed circuit in this report includes;
 - Rotary Encoders:
Rotary encoders are sensors used to measure the position of a rotating object. Gray code is often employed in rotary encoders because it reduces the chance of errors when transitioning between values.
 - Robotics and Motion Control:
In applications where precise motion control is essential, such as robotics, Gray code is used to represent positions.
 - Digital Signal Processing (DSP):
In certain DSP applications, Gray code is used for signal processing or encoding. A binary-to-gray code converter can be integrated into DSP systems to handle data in Gray code format.
 - Telecommunications:
In digital communication systems, Gray code is used in certain modulation and encoding techniques.
- Using the MICROWIND and DSCH software, a combination of CMOS was assembled to form an XOR gate, which in turn by combination with two inverters formed a triumphant working model of a 2 bit Binary to Gray code converter through successful and optimum utilization of its' truth table, gate level and transistor level schematic diagram and a stick diagram for an efficient CMOS implementation which would provide an unordered series of Gray encoded bits in result as a output of four possible combination of binary bits.